
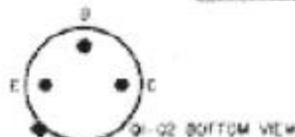


Push-button switch is behind circuit board. Transformer (right) is held to board by soldering the mounting tabs to clip clips. Battery can be attached to U-section of MiniBox with tape or standard holder. Schematic is below. Potentiometer R1 is used to set output level of Tripler relative to guitar's output. With S1 in position shown, signal from guitar is fed unaltered to output jack. Be sure to connect T1 as shown.

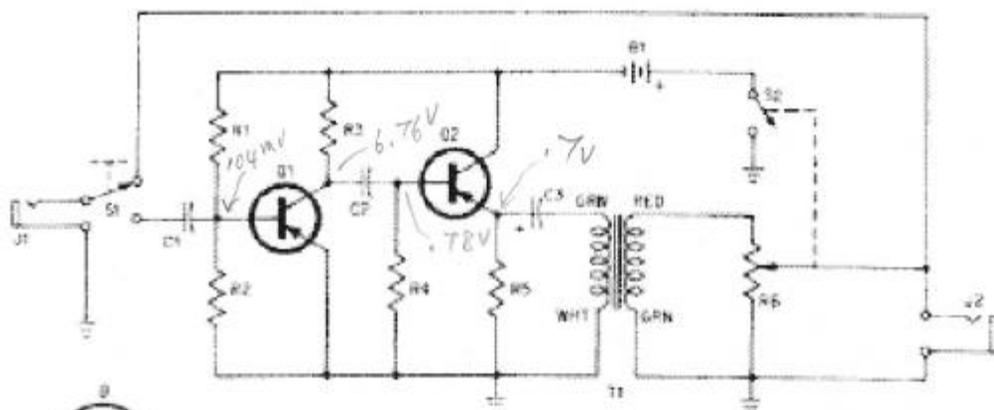

released, this switch stays in one position or the other until it is pushed a second time.

Operation

Connect the Tripler between the guitar and amplifier as you would any outboard accessory. Turn your amplifier on and set its volume control to a low level and set the tone control to mid-range. Turn the Tripler on and turn pot R6 to about three-quarters full clockwise. Depending on the position of S1 you should get either straight sound or emphasized treble sound. Step on the switch and start experimenting with the controls.

PARTS LIST

- B1—9 V battery
 - C1, C2—.001 μ f, 25 V or higher ceramic disc capacitor
 - C3—2 μ f, 15 V electrolytic capacitor
 - J1, J2—Phone jack
 - Q1, Q2—2N1414 transistor (GE, Motorola)
 - R1, R4—1 megohm, $\frac{1}{2}$ watt, 10% resistor
 - R2—22,000 ohm, $\frac{1}{2}$ watt, 10% resistor
 - R3, R6—10,000 ohm, $\frac{1}{2}$ watt, 10% resistor
 - R5—500,000 ohm, linear taper potentiometer with SPST switch
 - S1—SPDT pushpush switch (Carling 112 or equiv.)
 - S2—SPST switch on R6
 - T1—Transistor audio transformer, primary impedance: 200,000 ohms, secondary impedance: 1,000 ohms (Lafayette 99 T 6034) Max.— $5\frac{1}{2}$ x 2 x 2 $\frac{1}{2}$ -in. MiniBox, perforated circuit board
- The Carling 112 switch is available for \$2.50 contact from Teledac Electronics Corp., P.O. Box 313, Alton Manor Bld., Elmsford, N.Y. 11053. No foreign orders.